


Laboratory work 2

Studying of first- and second-order Typical Dynamic Elements parameters influence on their characteristics

2.1. Objective

Building of Simulink models of RC and RLC two-port circuits, obtaining their time and frequency characteristics for various R and C values, and studying influence of the circuit element parameter values on the transient behavior.

2.2 RC two-port circuit

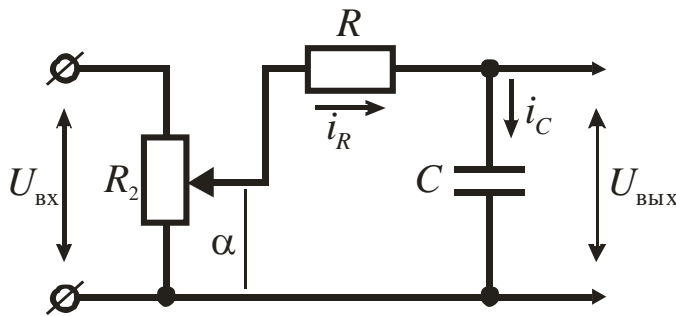

Equations describing the circuit operation

$$\begin{cases} i_R = i_C \\ i_C = C \frac{dU_{out}(t)}{dt} \\ i_R = \frac{[\alpha U_{in}(t) - U_{out}(t)]}{R} \end{cases} \quad (2.1)$$

$$U_{in} \rightarrow x$$

$$U_{out} \rightarrow y$$

Figure 2.1 – Electrical schematic of an RC two-port circuit

The structural algorithmic diagram represents the graphical presentation of differential equations written in operator form.

The operator form of differential equations (2.1) is:

$$\begin{cases} i_R(p) = i_C(p) & (1') \\ i_C(p) = CpU_{out}(p) & (2') \\ i_R(p) = \frac{1}{R}[\alpha U_{in}(p) - U_{out}(p)] & (3') \end{cases} \quad (2.2)$$

Transfer function is defined as ratio of output $U_{out}(p)$ and input $U_{in}(p)$ signals in operational form:

$$W(p) = \frac{y(p)}{x(p)} = \frac{U_{out}(p)}{U_{in}(p)} = \frac{\sum_{l=0}^m b_l p^l}{\sum_{k=0}^m a_k p^k} \quad (2.3)$$

Let us obtain the expression linking these parameters by substituting equations (2') and (3') to equation (1'):

$$\frac{1}{R}[\alpha U_{in}(p) - U_{out}(p)] = CpU_{out}(p) \quad (2.4)$$

The expression describing the output parameter is written on the left, while the expression describing the input parameter is on written on the right:

$$CpU_{out}(p) + \frac{1}{R}U_{out}(p) = \frac{1}{R}\alpha U_{in}(p), \quad (2.5)$$

or:

$$[(C \cdot R)p + 1]U_{out}(p) = \alpha U_{in}(p). \quad (2.6)$$

Consequently, the transfer function of the *RC* circuit considered is

$$W(p) = \frac{U_{out}(p)}{U_{in}(p)} = \frac{\alpha}{(R \cdot C)p + 1} \quad (2.7)$$

The transfer function obtained shows that the considered *RC* two-port circuit is a first-order aperiodic dynamic element. Action of *R* and *C* values on its dynamic mode can be studied via Simulink model shown in Fig. 2.2.

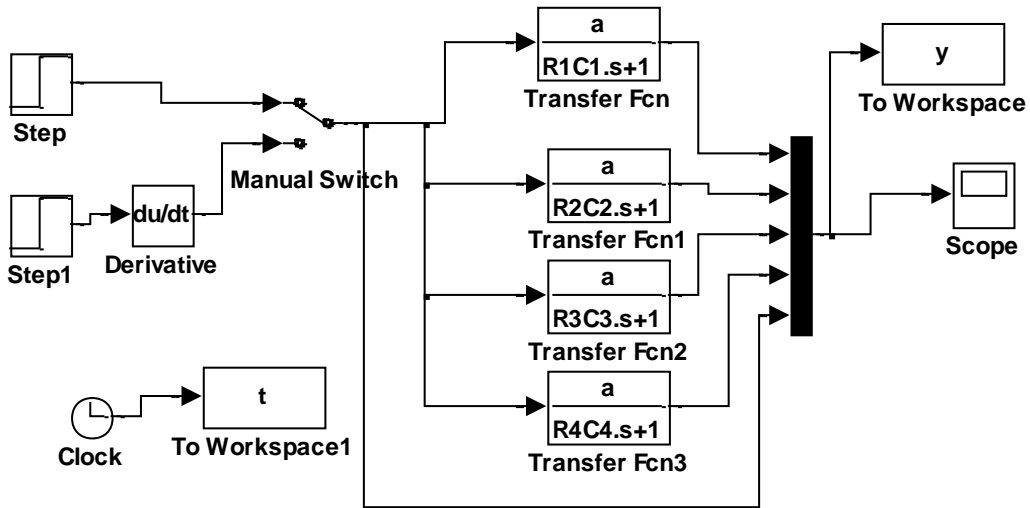


Figure 2.2 – Simulink model for studying dynamic behavior of RC two-port circuit versus resistance and capacitance values

2.3 RLC two-port circuit

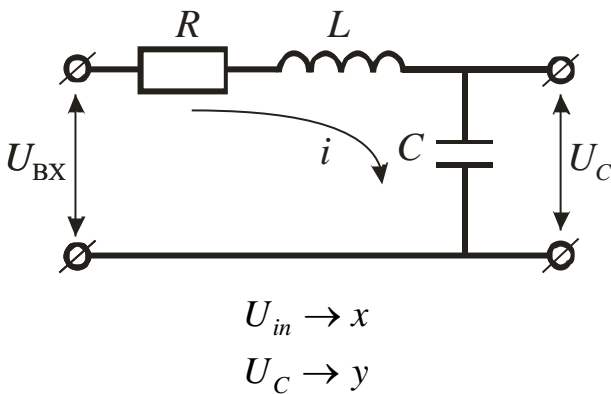


Figure 2.3 - Electrical schematic of an RCL two-port circuit

Equations describing the circuit operation

$$\begin{cases}
 U_R = R \cdot i \\
 U_C = \frac{1}{C} \int i \cdot dt \\
 U_L = L \cdot \frac{di}{dt} \\
 U_{in} = U_R + U_L + U_C = \\
 \quad = R \cdot i + L \cdot \frac{di}{dt} + \frac{1}{C} \int i \cdot dt
 \end{cases} \quad (2.8)$$

To obtain the expression containing only input voltage $U_{in}(t)$ and output voltage $U_C(t)$, let us write equations (2.8) in the operator form and make required transformations:

$$\begin{cases}
 U_R(p) = R \cdot i(p) & (1') \\
 U_C(p) = \frac{1}{Cp} i(p) & (2') \\
 U_L(p) = Lpi(p) & (3') \\
 U_{in}(p) = U_R(p) + U_L(p) + U_C(p) = \\
 \quad = Ri(p) + Lpi(p) + \frac{1}{Cp} i(p) & (4')
 \end{cases} \quad (2.9)$$

From equation (2'), current $i(p)$ can be expressed with $U_C(p)$:

$$i(p) = CpU_C(p). \quad (2.10)$$

Substituting (2.10) to equations (1'), (3') and (4'), we obtain

$$\begin{aligned} U_{in}(p) &= (R \cdot C)pU_C(p) + (L \cdot C)p^2U_C(p) + U_C(p) = \\ &= [(L \cdot C)p^2 + (R \cdot C)p + 1]U_C(p) \end{aligned} \quad (2.11)$$

The transfer function is ratio of output voltage $U_C(p)$ and input voltage $U_{in}(p)$ in operational form:

$$W(p) = \frac{U_C(p)}{U_{in}(p)} = \frac{1}{(L \cdot C)p^2 + (R \cdot C)p + 1} \quad (2.12)$$

The transfer function obtained shows that the considered RLC two-port circuit is a second-order dynamic element. Its transient mode behavior (either aperiodic or oscillatory) defining the type of the dynamic link depends on the parameters of the circuit elements.

Action of R , L , and C values on the circuit dynamic mode can be studied via Simulink model shown in Fig. 2.4.

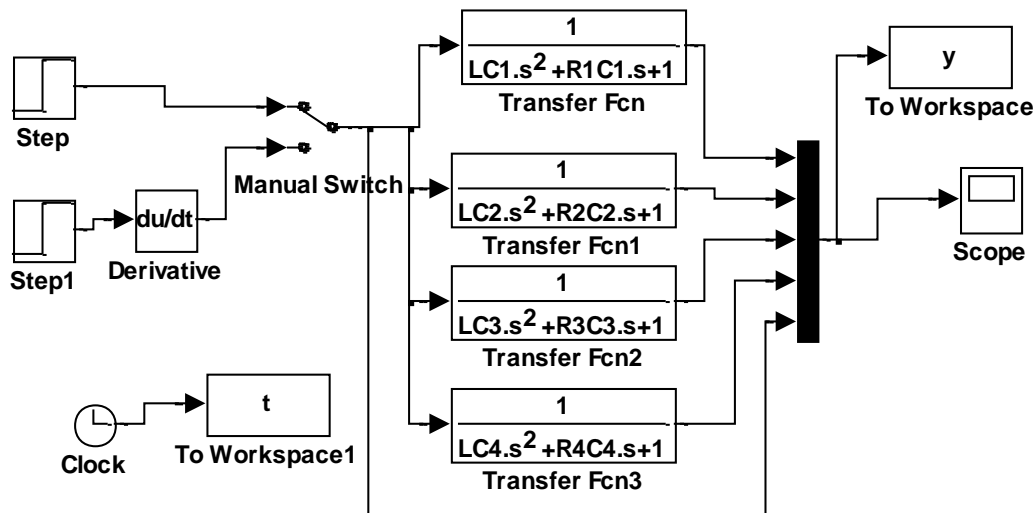


Figure 2.4 – Simulink model for studying dynamic behavior of RLC two-port circuit versus resistance, inductance and capacitance values

2.4 Assignment

Build Simulink models of RC and RLC circuits, obtain their time and frequency characteristics for different values of the circuit element parameters. Obtain their dynamic equations,

transfer functions, and complex gains. Analyze dynamic behavior of the considered two-port *RC* and *RLC* circuits versus the circuit element parameter values specified in table 2.1 according to the variant.

Table 2.1 Variants of the two-port circuit element parameter values

вариант	α	L, H	$R1, \Omega$	$R2, \Omega$	$R3, \Omega$	$R4, \Omega$	$C1, \text{F}$	$C2, \text{F}$	$C3, \text{F}$	$C4, \text{F}$
1	0.8	0.28	720	480	180	180	$8.20 \cdot 10^{-5}$	$8.20 \cdot 10^{-6}$	0.00047	$8.20 \cdot 10^{-6}$
2	0.2	0.12	750	510	340	121	$4.70 \cdot 10^{-5}$	$4.70 \cdot 10^{-6}$	$4.20 \cdot 10^{-6}$	$8.20 \cdot 10^{-6}$
3	0.15	0.32	750	630	340	200	$1.20 \cdot 10^{-6}$	$1.20 \cdot 10^{-5}$	$4.70 \cdot 10^{-6}$	$8.20 \cdot 10^{-6}$
4	0.4	0.32	750	330	510	130	$1.20 \cdot 10^{-6}$	$1.20 \cdot 10^{-5}$	$4.70 \cdot 10^{-6}$	$8.20 \cdot 10^{-6}$
5	0.85	0.45	750	750	620	130	$4.20 \cdot 10^{-5}$	$8.20 \cdot 10^{-6}$	$4.70 \cdot 10^{-6}$	$6.20 \cdot 10^{-6}$
6	0.5	0.24	470	390	430	130	$4.20 \cdot 10^{-5}$	$1.20 \cdot 10^{-5}$	$4.70 \cdot 10^{-6}$	$8.20 \cdot 10^{-6}$
7	0.25	0.34	330	820	510	1580	$2.20 \cdot 10^{-6}$	$1.20 \cdot 10^{-5}$	$4.70 \cdot 10^{-6}$	$8.20 \cdot 10^{-6}$
8	0.1	0.12	330	470	100	300	$2.20 \cdot 10^{-6}$	$1.20 \cdot 10^{-5}$	$4.70 \cdot 10^{-5}$	$4.70 \cdot 10^{-5}$
9	0.9	0.85	510	470	430	820	$8.20 \cdot 10^{-5}$	$3.30 \cdot 10^{-5}$	$1.80 \cdot 10^{-5}$	$4.70 \cdot 10^{-5}$
10	0.75	0.55	470	470	360	680	$4.20 \cdot 10^{-5}$	$3.30 \cdot 10^{-6}$	$1.80 \cdot 10^{-5}$	$4.70 \cdot 10^{-5}$

Appendix
Plotting frequency characteristics for second-order TDE in Matlab

Dynamic equation of a second-order TDE is

$$T^2 \frac{d^2 y(t)}{dt^2} + 2\xi T \frac{dy(t)}{dt} = kx(t) \quad (2.13)$$

and the transfer function is

$$W(s) = \frac{k}{T^2 s^2 + 2\xi T s + 1}, \quad (2.14)$$

where k is transfer coefficient; T is time constant; ξ is damping factor.

Value of damping factor ξ specifies the transient behavior of the TDE (fig. 2.5):

$\xi \geq 1$ is characteristic of aperiodic transient;

$\xi < 1$ is characteristic of oscillatory transient.

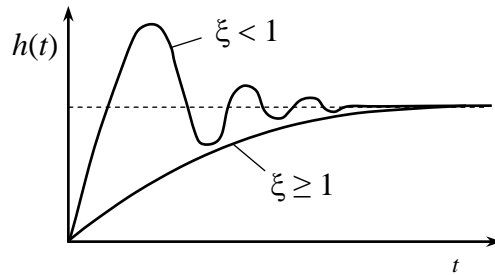


Figure 2.5 – Transient characteristics of 2nd –order TDE versus damping factor ξ

Unit step response (Heaviside response) is

$$h(t) = k[1 - Ae^{-\alpha t} \sin(\omega t + \varphi)],$$

where A and φ are integration constants determined under zero initial conditions,

$$A = 1/\sqrt{1-\xi^2}; \quad \varphi = \arcsin \sqrt{1-\xi^2};$$

Unit impulse response () is

$$w(t) = h'(t).$$

Time constant T and damping factor ξ can be found from frequency characteristics. Frequency characteristics are found using complex transfer function $W(j\omega)$

$$W(j\omega) = W(s)|_{s=j\omega} = \frac{k}{T^2 (j\omega)^2 + 2\xi T(j\omega) + 1} \quad (2.15)$$

or

$$W(j\omega) = W(s)|_{s=j\omega} = \frac{k(1-T^2\omega^2)}{(1-T^2\omega^2)^2 + 4\xi^2 T^2 \omega^2} - j \frac{2k\xi T\omega}{(1-T^2\omega^2)^2 + 4\xi^2 T^2 \omega^2} \quad (2.16)$$

Second-order TDE (aperiodic transient)

The initial parameters of the 2nd-order TDE are given in table 2.2.

Table 2.2 – Parameters of *RLC*-circuit (see fig. 2.3)

k	L, H	R, Ω	C, F
0.8	0.28	720	$8.20 \cdot 10^{-5}$


Transfer function of this dynamic element after substituting values of the *RLC*-circuit parameters to (2.12)

$$W(p) = W(s)|_{s=p} = \frac{0.8}{0.28 \cdot 8.2 \cdot 10^{-5} p^2 + 720 \cdot 8.2 \cdot 10^{-5} p + 1}$$

According to (2.14), time constant T is equal to square root of the coefficient at p^2 , that is $T = (0.28 \cdot 8.2 \cdot 10^{-5})^{0.5} = 0.0048$.

Damping factor ξ is equal to the coefficient at p divided by double time constant, that is $\xi = (720 \cdot 8.2 \cdot 10^{-5}) / (2 \cdot 0.0048) = 6.15$, which is > 1 , therefore the *RLC*-circuit with the considered parameters behaves as a 2nd-order aperiodic TDE.

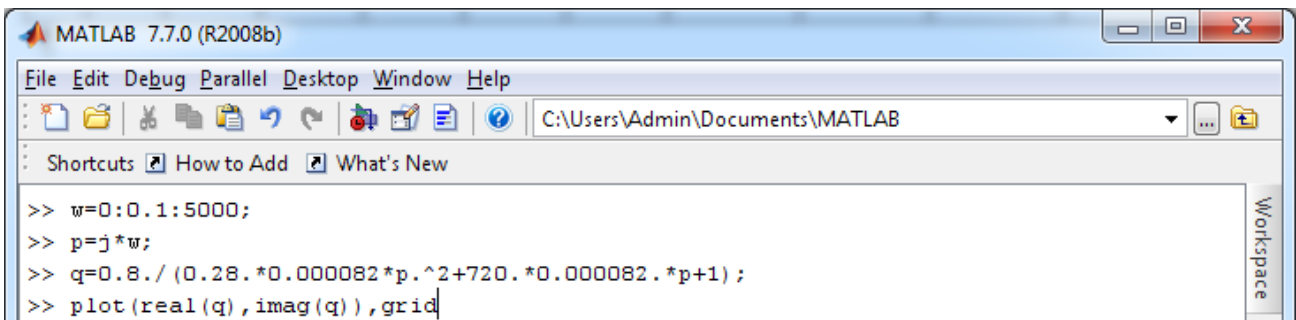To plot frequency characteristics, the expression for the transfer function $W(p)$ must be written in **Command window** and converted to complex transfer function $W(j\omega)$. For this, the following commands are introduced:



```
>> w=0:0.1:5000;  
>> p=j*w;  
>> q=0.8./ (0.28.*0.000082*p.^2+720.*0.000082.*p+1);  
>> plot(real(q),imag(q)),grid
```

Matlab command **plot(real(q),imag(q)),grid** allows plotting amplitude-phase frequency characteristic:

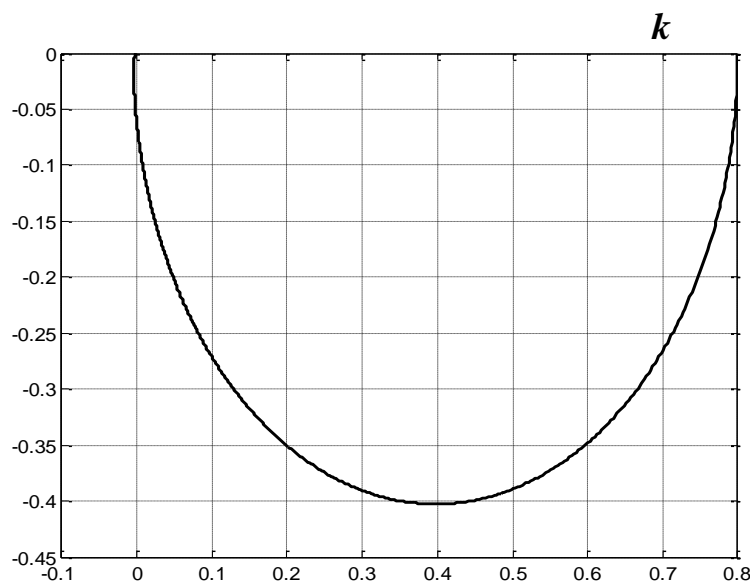


Figure 2.6 – Amplitude-phase frequency characteristic

Amplitude-phase frequency characteristic is the hodograph of the complex transfer function $W(j\omega)$.

The $W(j\omega)$ hodograph of a 2nd-order TDE starts at point $[k,0]$ at $\omega = 0$, which allows determining the transfer coefficient k in case the characteristic is obtained experimentally and the parameter is not known.

For the TDE studied, k is 0.8 and the characteristic starts at point $[0.8,0]$.

The hodograph (or amplitude-phase frequency characteristic) crosses Im -axis at point $[0, -k/(2\xi)]$. Hence it is also possible to determine damping factor ξ from the amplitude-phase frequency characteristic

For the TDE studied, $-0.8/(2\xi) = -0.065$, therefore $\xi = 0.8/(2*0.065) = 6.15$, which exactly coincides with the computed value.

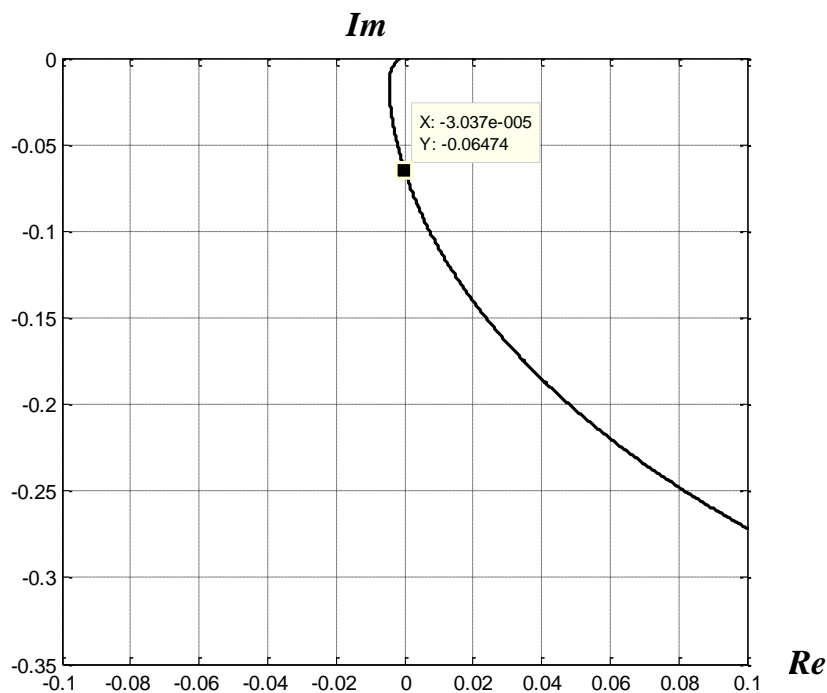


Figure 2.7 – Crosspoint of the amplitude-phase frequency characteristic and Im -axis

Matlab command `plot(w,real(q)),grid` allows plotting real frequency characteristic $Re(\omega)$.

```

MATLAB 7.7.0 (R2008b)
File Edit Debug Parallel Desktop Window Help
C:\Users\Admin\Documents\MATLAB
Shortcuts How to Add What's New
>> w=0:0.1:5000;
>> p=j*w;
>> q=0.8./ (0.28.*0.000082*p.^2+720.*0.000082.*p+1);
>> plot(real(q), imag(q), grid)
>> plot(w, real(q), grid)
Workspace

```

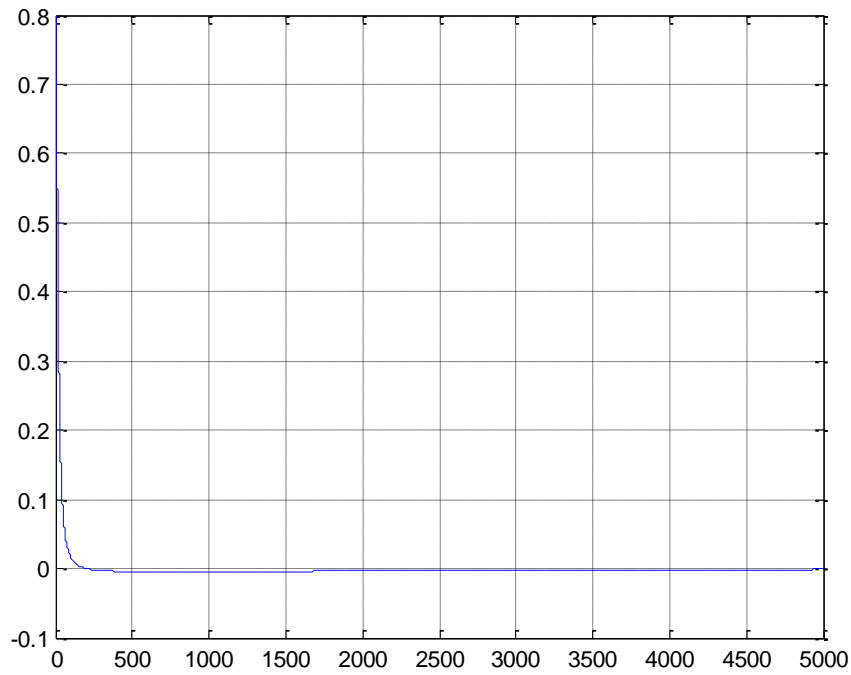



Figure 2.8 – Real frequency characteristic $\text{Re}(\omega)$

Figure 2.9 shows the low-frequency domain of $\text{Re}(\omega)$. The real frequency characteristic of a 2nd-order TDE starts at k at $\omega = 0$, which makes it possible to determine the transfer coefficient of a 2nd-order TDE in case the parameter is unknown.

For the TDE studied the transfer coefficient, $k = 0.8$ and $\text{Re}(\omega)$ starts at 0.8.

At frequency $\omega = 1/T$, the real frequency characteristic of a 2nd-order TDE crosses ω -axis and, hence, the point of $\text{Re}(\omega) = 0$ allows determining time constant T .

For the TDE studied, $\text{Re}(\omega) = 0$ at frequency $\omega \approx 200 \text{ s}^{-1}$. Consequently, $T = 1/200 = 0.005$, which is in good agreement with the computed value 0.0048.

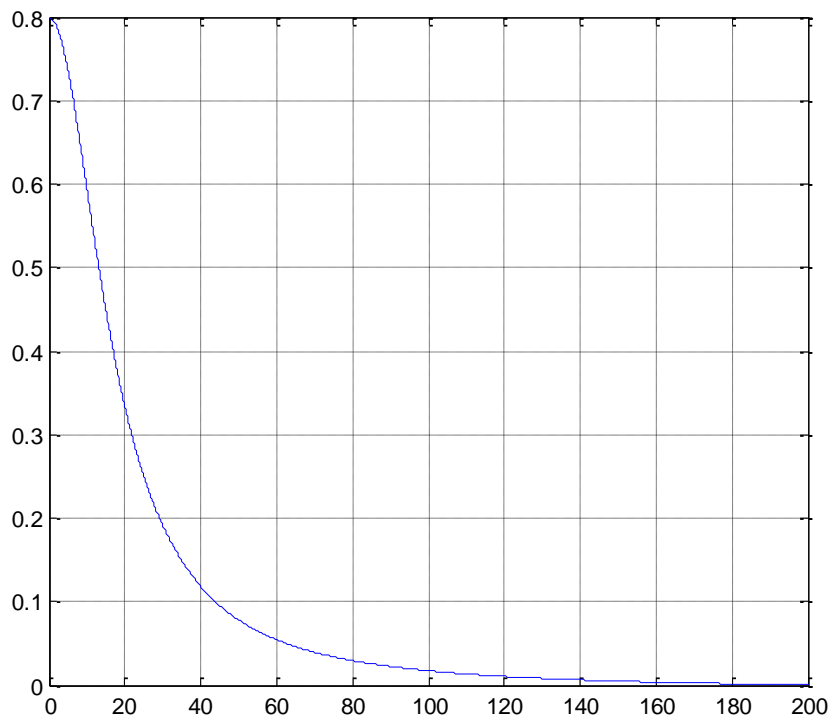


Figure 2.9 – Low-frequency domain of $\text{Re}(\omega)$

Matlab command `plot(w,imag(q)),grid` allows plotting imaginary frequency characteristic $\text{Im}(\omega)$.

```

MATLAB 7.7.0 (R2008b)
File Edit Debug Parallel Desktop Window Help
C:\Users\Admin\Documents\MATLAB
Shortcuts How to Add What's New
Workspace
>> w=0:0.1:5000;
>> p=j*w;
>> q=0.8./ (0.28.*0.000082*p.^2+720.*0.000082.*p+1) ;
>> plot(real(q),imag(q),grid)
>> plot(w,real(q),grid)
>> plot(w,imag(q),grid)

```

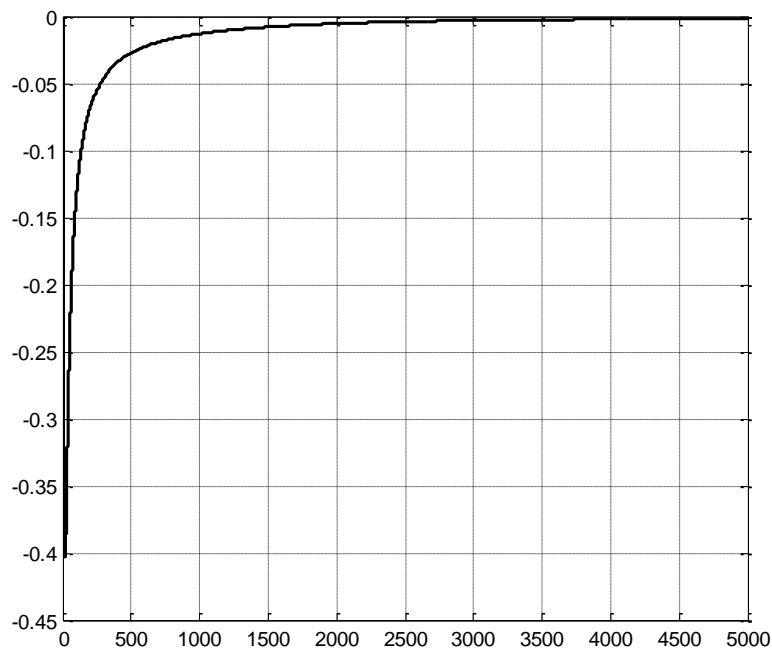


Figure 2.10 – Imaginary frequency characteristic $\text{Im}(\omega)$

The characteristic helps determine time constant T (if the damping factor ξ is known) or damping factor ξ (if the time constant is known) of a 2nd-order TDE.

At frequency $\omega = 1/T$, $\text{Im}(\omega)$ reaches the level of $-k/(2\xi)$.

Figure 2.11 presents the low-frequency domain to show minimum of $\text{Im}(\omega)$ and level of $-k/(2\xi)$.

For given ξ , according to the graph, at the level of $-0.8/(2*6.15) = -0.065$, frequency is approximately 220 s^{-1} , therefore $T = 1/220 = 0.0045$, which is quite close to the computed value of 0.0048.

For given T , at frequency $\omega = 1/0.0048 = 208 \text{ s}^{-1}$, $-0.8/(2*\xi) \approx -0.067$ according to the graph. Therefore, $\xi = 0.8/(2*0.067) = 5.97 (\approx 6)$, which is in acceptable agreement with the computed value of 6.15 (≈ 6).

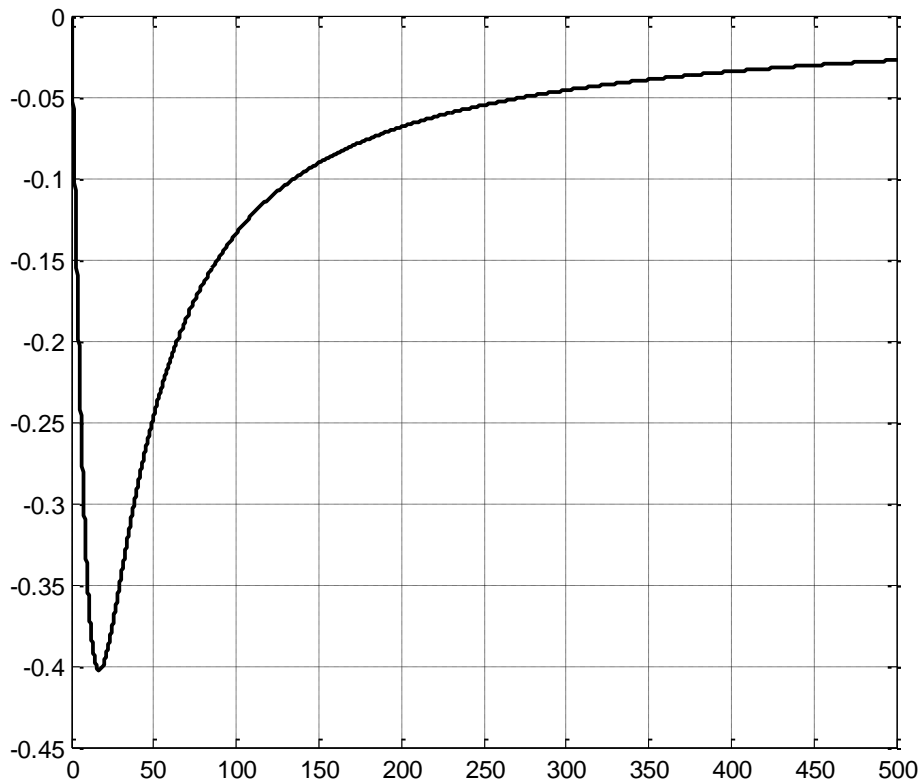


Figure 2.11 – Low frequency domain of $\text{Im}(\omega)$

Matlab command **plot(w,abs(q)),grid** allows plotting magnitude frequency characteristic $A(\omega)$.

```

MATLAB 7.7.0 (R2008b)
File Edit Debug Parallel Desktop Window Help
C:\Users\Admin\Documents\MATLAB
Shortcuts How to Add What's New
Workspace
>> w=0:0.1:5000;
>> p=j*w;
>> q=0.8./ (0.28.*0.000082*p.^2+720.*0.000082.*p+1) ;
>> plot(real(q), imag(q), grid)
>> plot(w, real(q), grid)
>> plot(w, imag(q), grid)
>> plot(real(q), imag(q), grid)
>> plot(w, abs(q), grid)

```

Magnitude frequency characteristic $A(\omega)$ helps determine transfer coefficient k and time constant T in case the characteristic is obtained experimentally and the parameters of the equipment that is modelled as a 2nd-order TDE is unknown.

$A(\omega)$ starts at k , that is at $\omega = 0$, $A(0) = k$, which makes it possible to specify the transfer coefficient.

At $\omega = 1/T$, the curve declines to the level of $k/(2\xi)$ so time constant T can be found.


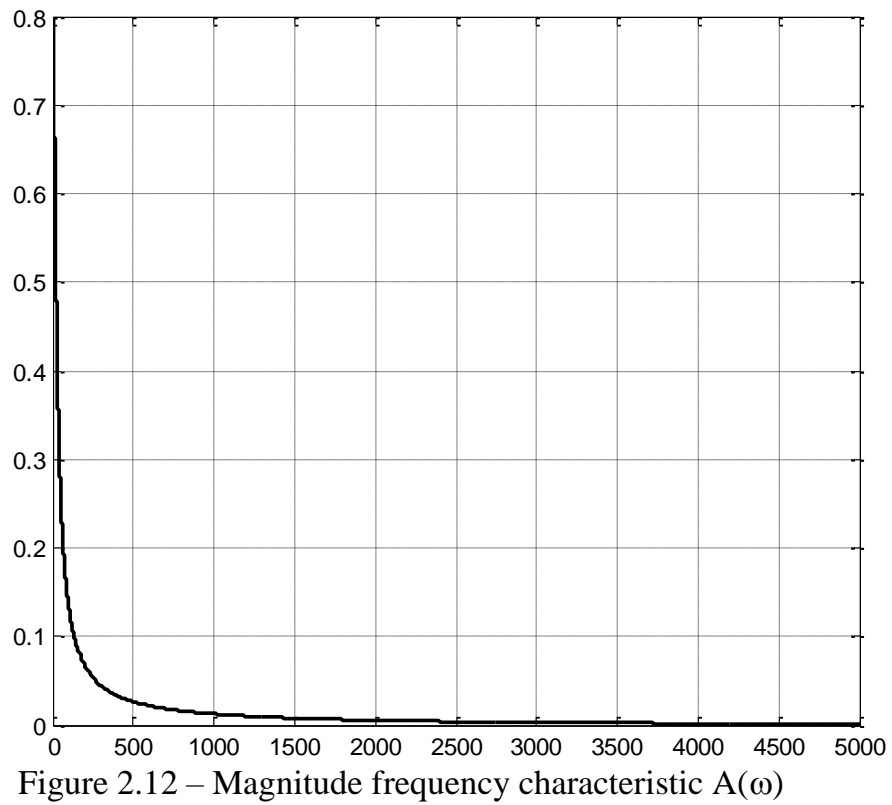


Figure 2.13 presents the low-frequency domain of $A(\omega)$.

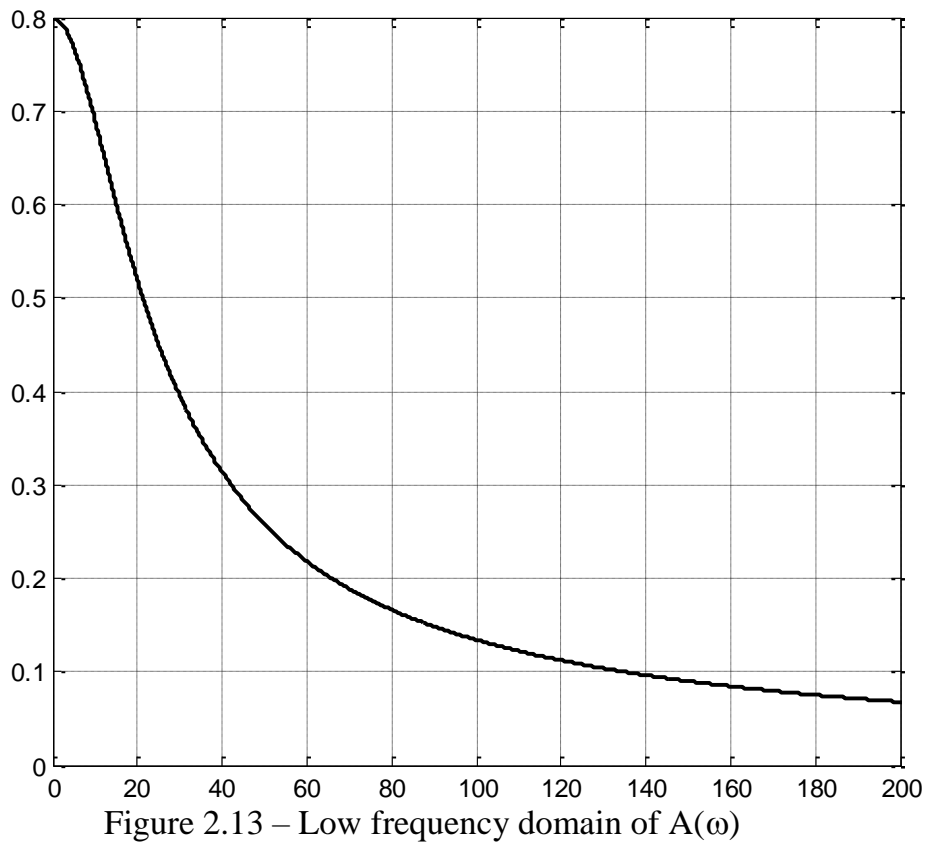

For the TDE studied, at $\omega = 0$ $A(0) = 0.8$.

At the level of $0.8/(2 \cdot 6.15) = 0.065$, $\omega \approx 200 \text{ s}^{-1}$. Consequently, $T = 1/200 = 0.005$, which is quite close to the computed value 0.0048.

Matlab command `bode([b0 b1 ... bm],[a0 a1 ... am]),grid` (where $b_0 b_1 \dots b_m$ and $a_0 a_1 \dots a_m$ are, correspondingly, coefficients of the numerator and denominator of the transfer function) allows plotting Bode magnitude $L(\omega)$ and phase $\phi(\omega)$ plots.

```

MATLAB 7.7.0 (R2008b)
File Edit Debug Parallel Desktop Window Help
C:\Users\Admin\Documents\MATLAB
Shortcuts How to Add What's New
Workspace

>> w=0:0.1:5000;
>> p=j*w;
>> q=0.8./(0.28.*0.000082*p.^2+720.*0.000082.*p+1);
>> plot(real(q),imag(q),grid)
>> plot(w,real(q),grid)
>> plot(w,imag(q),grid)
>> plot(real(q),imag(q),grid)
>> plot(w,abs(q),grid)
>> bode([0.8],[0.28*0.000082 720*0.000082 1]),grid
??? bode([0.8],[0.28*0.000082 720*0.000082 1]),grid
    |
Error: Unbalanced or unexpected parenthesis or bracket.

>> bode([0.8],[0.28*0.000082 720*0.000082 1]),grid
>> |

```

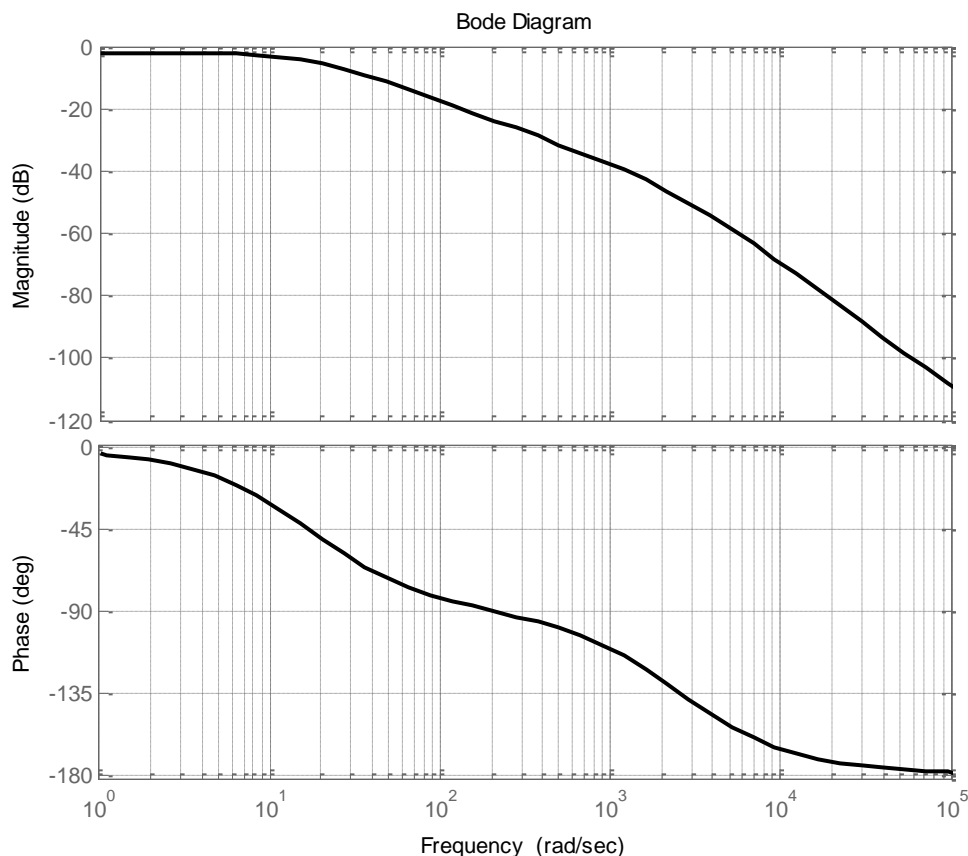


Figure 2.14 – Magnitude frequency characteristic $A(\omega)$

The Bode magnitude plot demonstrates two slope breaks and the Bode phase plot has two waves, which is characteristic of a 2nd –order dynamic element with aperiodic transient and quite a high damping factor, which is the case considered.

The first break frequency ω_{b1} of $L(\omega)$ coincides with frequency $\omega_{.45}$ of $\varphi(\omega)$ crossing the level of -45° .

The other break frequency ω_{b2} of $L(\omega)$ coincides with frequency $\omega_{.135}$ of $\varphi(\omega)$ crossing the level of -135 .

A 2nd-order aperiodic TDE (A-II TDE) is a complex dynamic element comprising two 1st-order aperiodic TDEs (A-I TDEs) connected in series, so the transfer function of A-II TDE (2.14) is product of transfer functions of the two A-I TDEs:

$$W(s)_{A-II} = W(s)_{1A-I} \cdot W(s)_{2A-I} = \frac{1}{T_1s + 1} \cdot \frac{k}{T_2s + 1}, \quad (2.17a)$$

or

$$W(s)_{A-II} = \frac{k}{T^2s^2 + 2\xi Ts + 1} = \frac{1}{T_1s + 1} \cdot \frac{k}{T_2s + 1} = \frac{k}{(T_1 \cdot T_2)s^2 + (T_1 + T_2)s + 1}, \quad (2.17b)$$

where T_1 is time coefficient of one 1st-order TDE and T_2 is time constant of the other 1st-order TDE.

From (2.17), T_1 and T_2 related to time constant T and damping factor ξ of the 2nd-order TDE:

$$T_1 \cdot T_2 = T \quad \text{and} \quad T_1 + T_2 = 2\xi T$$

T_1 and T_2 can be found from Bode plots as $T_1 = 1/\omega_{b1}$ and $T_2 = 1/\omega_{b2}$.

For the A-II TDE studied

$$\omega_{b1} = \omega_{.45} \approx 18, \text{ so } T_1 = 1/18 = 0.0556$$

$$\omega_{b2} = \omega_{.135} \approx 2400, \text{ so } T_2 = 1/2400 = 0.000417$$

$$T_1 \cdot T_2 = 0.0556 \cdot 0.000417 = 0,00002318$$

$$\text{In the 2}^{\text{nd}}\text{-order TDE studied, } T^2 = L \cdot C = (0.28 \cdot 8.2 \cdot 10^{-5}) = 0.00002296$$

$$T_1 + T_2 = 0.0556 + 0.000417 = 0,056017$$

$$\text{In the 2}^{\text{nd}}\text{-order TDE studied, } 2\xi T = R \cdot C = (720 \cdot 8.2 \cdot 10^{-5}) = 0.05904$$

As we can see, results of the calculation and the simulation are in good agreement, which verifies the correctness of the characteristics plotted.

Second-order TDE (oscillatory transient)

The initial parameters of the 2nd-order TDE are given in table 2.3.

Table 2.3 – Parameters of the *RCL*-circuit (fig. 2.3)

k	L, H	$R1, \Omega$	$C1, \text{F}$
0.8	0.28	180	$8.20 \cdot 10^{-6}$

Transfer function of this dynamic element after substituting values of the *RCL*-circuit parameters to (2.12) is

$$W(p) = W(s)|_{s=p} = \frac{0.8}{0.28 \cdot 8.2 \cdot 10^{-6} p^2 + 180 \cdot 8.2 \cdot 10^{-6} p + 1}$$

Time constant T is equal to square root of the coefficient at p^2 , that is
 $T = (0.28 \cdot 8.2 \cdot 10^{-6})^{0.5} = 0.0015$.

Damping factor ξ is equal to the coefficient at p divided by double time constant, that is
 $\xi = (180 \cdot 8.2 \cdot 10^{-6}) / (2 \cdot 0.0015) = 0.492$, which is < 1 , therefore the *RLC*-circuit with the considered parameters behaves as a 2nd-order oscillatory TDE.

To plot frequency characteristics, the above-described **Matlab** commands are gradually applied to the considered TDE.

```
>> w=0:0.1:5000;  
>> p=j*w;  
>> q=0.8./ (0.28.*0.0000082*p.^2+180.*0.0000082.*p+1);  
>> plot(real(q),imag(q),grid)  
>> plot(w,real(q),grid)  
>> plot(w,imag(q),grid)  
>> plot(w,abs(q),grid)  
>> bode([0.8],[0.28*0.0000082 180*0.0000082 1]),grid
```

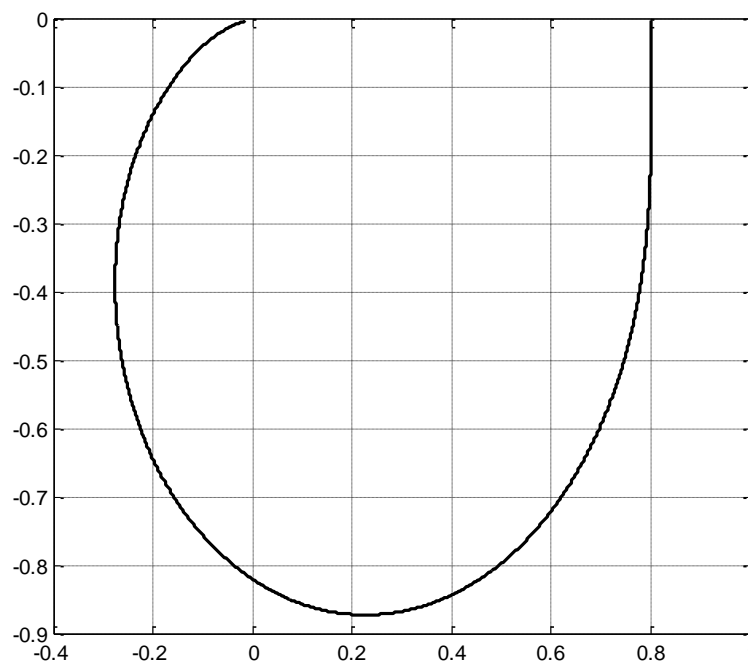


Figure 2.15 – Amplitude-phase frequency characteristic $W(j\omega)$

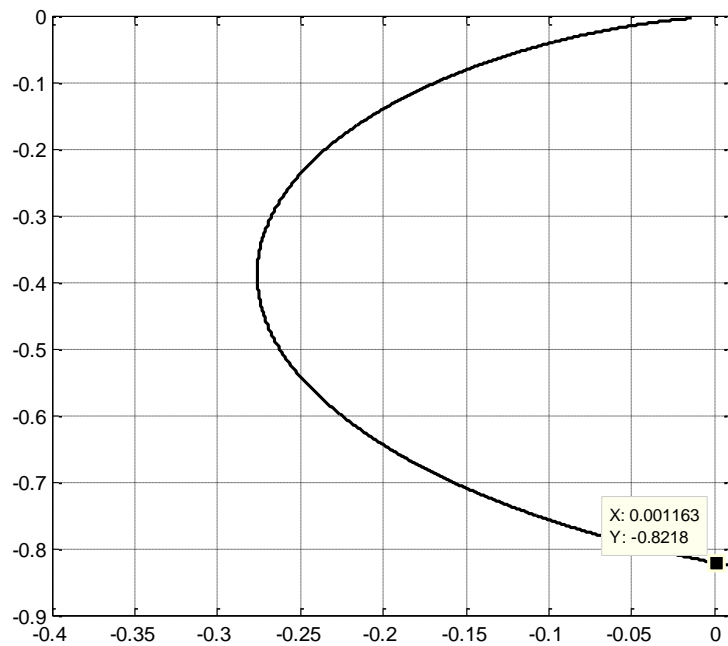


Figure 2.16 – Zoomed-up view of the amplitude-phase frequency characteristic crossing with *Im*-axis

$-0.8/(2\xi)=-0.822$, therefore damping factor $\xi=0.8/(2*0.822)=0.49$, which is equal to the computed value.

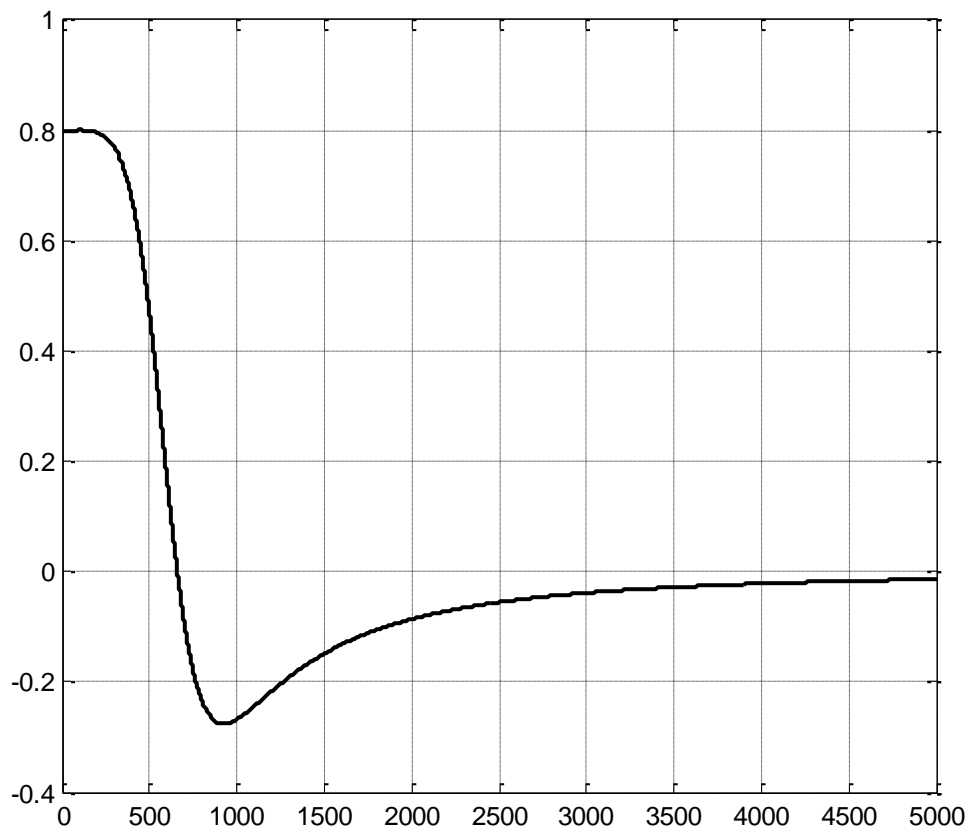


Figure 2.17 – Real frequency characteristic $Re(\omega)$

At frequency $\omega=1/T$, $\text{Re}(\omega) = 0$. The characteristic crosses ω -axis at frequency $\omega \approx 600 \text{ s}^{-1}$. Consequently, $T=1/600=0.00167$, which is close to the computed value 0.0015.

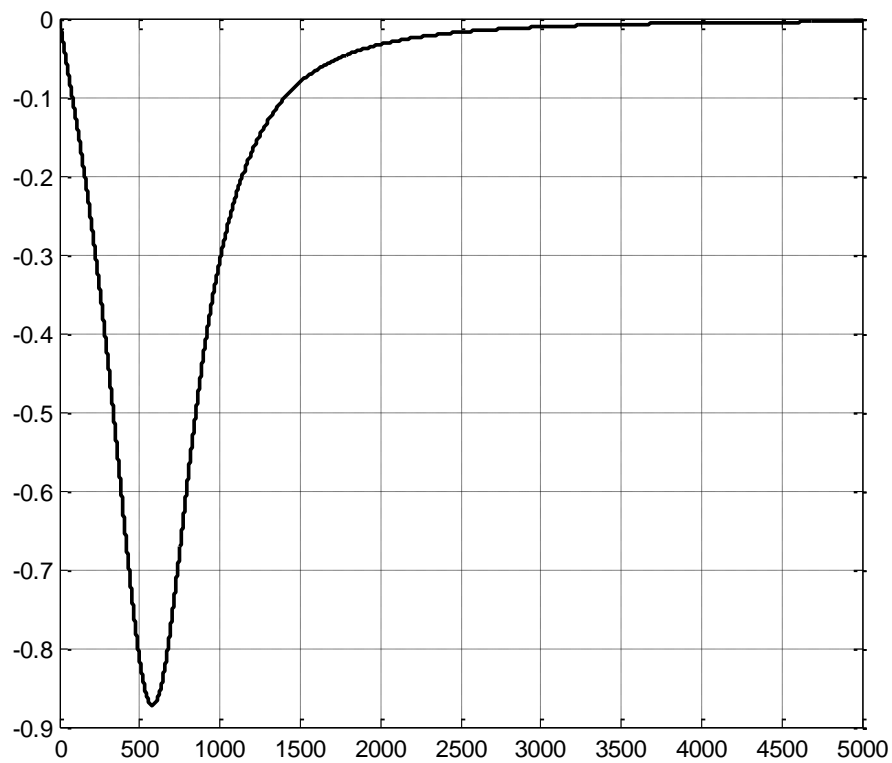


Figure 2.18 – Imaginary frequency characteristic $\text{Im}(\omega)$

At frequency $\omega=1/T$, $\text{Im}(\omega)$ crosses the level of $-k/(2\xi)$.

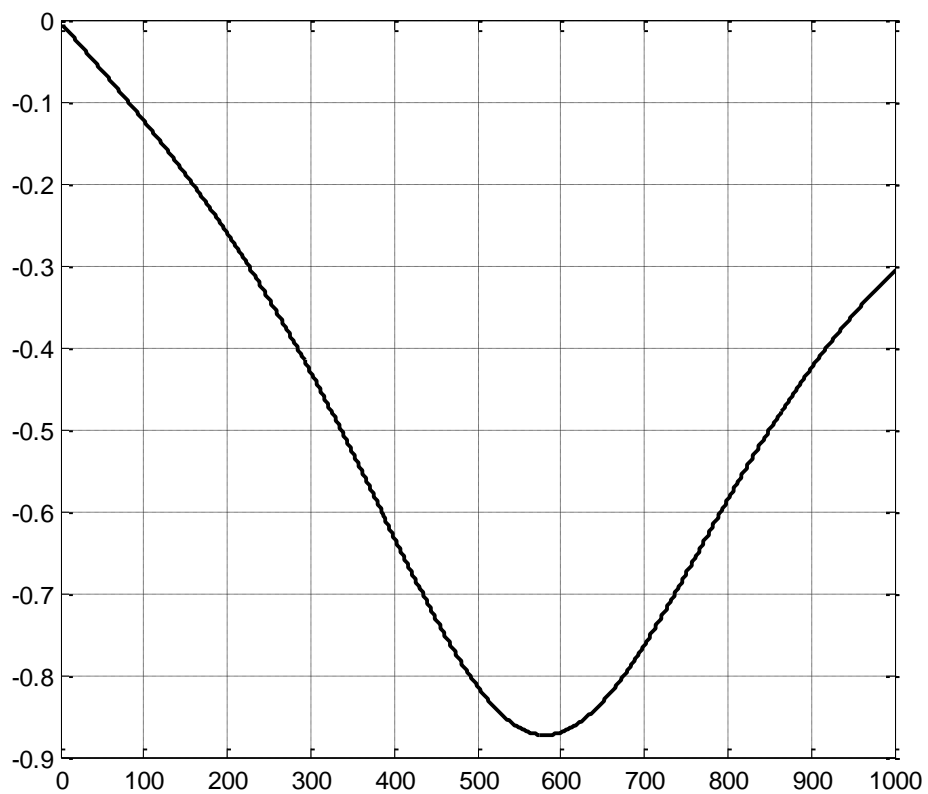


Figure 2.19 – Zoomed-up view of $\text{Im}(\omega)$ minimum

According to the graph, at the level of $-0.8/(2*0.49)=-0.816$, frequency is approximately 510 s^{-1} , therefore $T=1/510=0.00196$, which is quite close to the computed value of 0.0015.

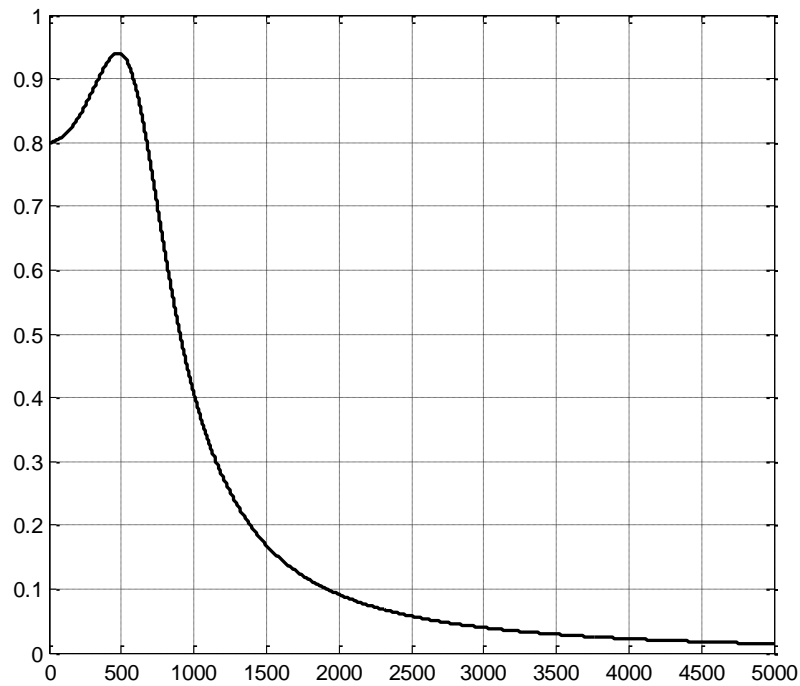


Figure 2.20 – Magnitude frequency characteristic $A(\omega)$

The characteristic demonstrates a resonance, which is typical of a 2nd-order oscillatory DE (or a control system of the kind) with damping factor $\xi < 0.7$. In the considered case, $\xi=0.492$. At the resonance frequency $\omega_{\text{res}} = \frac{\sqrt{1-2\xi^2}}{T}$, $A(\omega)$ reaches maximum of

$$A(\omega_{\text{res}}) = \frac{k}{2\xi\sqrt{1-\xi^2}} .$$

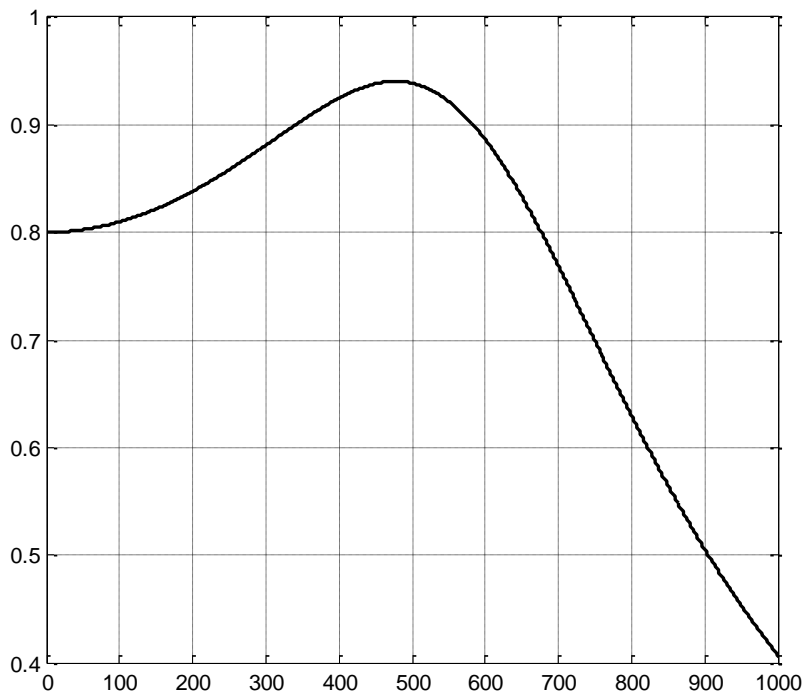


Figure 2.21 – Zoomed-up view of the $A(\omega)$ resonance

For the TDE studied, $\omega_{\text{res}} = \frac{\sqrt{1 - 2 \cdot 0.49^2}}{0.0015} = 480 \text{ s}^{-1}$ and

$A(\omega_{\text{res}}) = \frac{0.8}{2 \cdot 0.49 \sqrt{1 - 0.49^2}} = 0.936$. The results obtained by calculation completely coincide with the characteristic plotted.

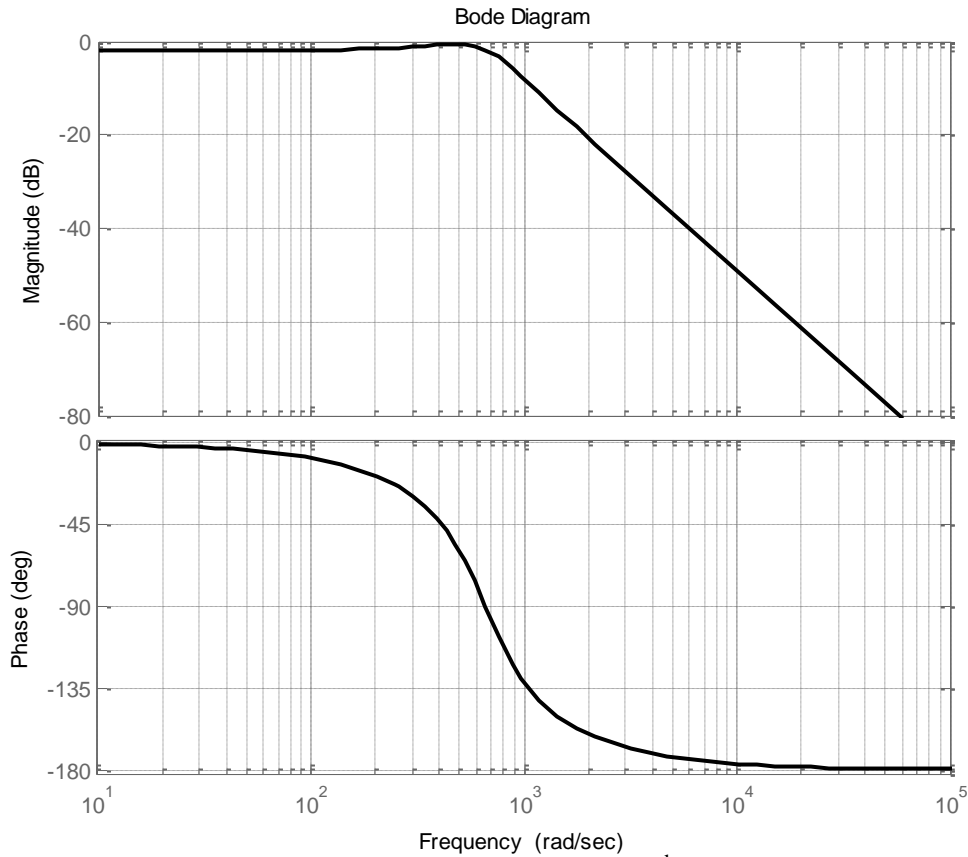


Figure 2.22 – Bode magnitude and phase plots for the 2nd-order oscillatory TDE studied. Bode magnitude plot also shows resonance at the frequency $\omega_{\text{res}} \approx 500 \text{ s}^{-1}$. The slope of the curve breaks only once from 0 dB/decade to -40 dB/decade, which is characteristic of a 2nd-order oscillatory TDE.

The break frequency $\omega_b \approx 630 \text{ s}^{-1}$ coincides with $\omega_{.90}$ which is the frequency of Bode phase plot crossing “-90” level, $\omega_b = \omega_{.90} \approx 630 \text{ s}^{-1}$.

Break frequency is opposite to time constant T , $\omega_b = 1/T$, therefore $T = 1/\omega_b$, and for the TDE studied $T = 1/630 = 0.00159$ against 0.0015 computed, which verifies the correctness of the characteristics plotted.